

# **OP-AMP BASED LISTENING BUG CIRCUIT DESIGN AND IMPLEMENTATION**



**ANALOG INTEGRATED CIRCUIT**

**A PROJECT REPORT**

*Submitted by*

**MATHESH M**

**MOTHIS S**

**SANJAI M**

*in partial fulfillment for the award of the degree*

*of*

**BACHELOR OF ENGINEERING**

*in*


**ELECTRONICS AND COMMUNICATION ENGINEERING**

**K.RAMAKRISHNAN COLLEGE OF TECHNOLOGY**

(An Autonomous Institution, Affiliated to Anna University Chennai and Approved by AICTE, New Delhi)

**SAMAYAPURAM, TIRUCHIRAPPALLI – 621 112**

**DECEMBER, 2024**

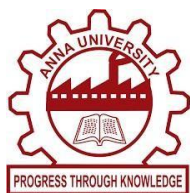

# **OP-AMP BASED LISTENING BUG CIRCUIT DESIGN AND IMPLEMENTATION**



**ANALOG INTEGRATED CIRCUIT**

**A PROJECT REPORT**

*Submitted by*

**MATHESH M**

**MOTHIS S**

**SANJAI M**

*in partial fulfillment for the award of the degree*

*of*

**BACHELOR OF ENGINEERING**

*in*

**ELECTRONICS AND COMMUNICATION ENGINEERING**

**K.RAMAKRISHNAN COLLEGE OF TECHNOLOGY**

(An Autonomous Institution, Affiliated to Anna University Chennai and Approved by AICTE, New Delhi)

**SAMAYAPURAM, TIRUCHIRAPPALLI – 621 112**

**DECEMBER, 2024**

**K. RAMAKRISHNAN COLLEGE OF TECHNOLOGY**  
**(AUTONOMOUS)**

**SAMAYAPURAM, TIRUCHIRAPPALLI– 621 112**

**BONAFIDE CERTIFICATE**

Certified that this project report titled “**OP-AMP BASED LISTENING BUG CIRCUIT DESIGN AND IMPLEMENTATION**” is the bonafide work of **MATHESH M (2303811710621063) , MOTHIS S (2303811710621071), SANJAI M (2303811710621095)** who carried out the project under my supervision. Certified further, that to the best of my knowledge the work reported herein does not form part of any other project report or dissertation on the basis of which a degree or award was conferred on an earlier occasion on this or any other candidate.

**SIGNATURE**

Dr. S. SYEDAKBAR, M.E., Ph.D.,

**HEAD OF THE DEPARTMENT**

Assistant Professor

Department of Electronics and  
Communication Engineering

K Ramakrishnan College of Technology  
(Autonomous)

Samayapuram – 621 112

**SIGNATURE**

Mrs. G. KEERTHANA, M.E.,

**SUPERVISOR**

Assistant Professor

Department of Electronics and  
Communication Engineering

K Ramakrishnan College of Technology  
(Autonomous)

Samayapuram – 621 112

Submitted for the viva-voce examination held on ...3-12-2024...

**INTERNAL EXAMINER**

**EXTERNAL EXAMINER**

## **DECLARATION**

We jointly declare that the project report on “**OP-AMP BASED LISTENING BUG CIRCUIT DESIGN AND IMPLEMENTATION**” is the result of original work done by us and best of our knowledge, similar work has not been submitted to “**ANNA UNIVERSITY CHENNAI**” for the requirement of Degree of **BACHELOR OF ENGINEERING**. This project report is submitted on the partial fulfillment of the requirement of the award of Degree of **BACHELOR OF ENGINEERING**.

**SIGNATURE**

---

**MATHESH M**

---

**MOTHIS S**

---

**SANJAI M**

Place :Samayapuram

Date : 3-12-2024

## ACKNOWLEDGEMENT

It is with great pride that we express our gratitude and in-debt to our institution “**K. Ramakrishnan College of Technology (Autonomous)**”, for providing us with the opportunity to do this project.

We are glad to credit honorable and admirable chairman **Dr. K. RAMAKRISHNAN, B.E.**, for having provided the facilities during the course of our study in college.

We would like to express our sincere thanks to our beloved Executive Director **Dr. S. KUPPUSAMY, MBA, Ph.D.**, for forwarding our project and offering adequate duration in completing our project.

We would like to thank **Dr. N. VASUDEVAN, M.Tech., Ph.D.**, Principal, who gave opportunity to frame the project with full satisfaction.

We whole heartedly thank **Dr. S. SYEDAKBAR, M.E., Ph.D.**, Head of the Department, Department of Electronics and Communication Engineering for providing his encouragement in pursuing this project.

We express our deep and sincere gratitude to our project guide, **Mrs.,G.KEERTHANA M.E.**, Assistant Professor, Department of Electronics and Communication Engineering, for his incalculable suggestions, creativity, assistance and patience which motivated us to carry out this project.

We wish to express my special thanks to the officials and Lab Technicians of our departments.

## **TABLE OF CONTENTS**

<b>CHAPTER NO</b>	<b>TITLE</b>	<b>PAGE NO</b>
<b>1</b>	<b>PROBLEM STATEMENT</b>	<b>1</b>
	1.1 WEAK SIGNAL AMPLIFICATION	1
	1.2 NOISE REDUCTION AND SIGNAL CLARITY	2
	1.3 POWER EFFICIENCY AND PORTABILITY	2
	1.4 COMPACTNESS AND DURABILITY	2
	1.5 BACKGROUND OF THE WORK	2
<b>2</b>	<b>DESIGN PROCEDURE OF BUG CIRCUIT</b>	<b>4</b>
	2.1 CIRCUIT DESIGN OF BUG CIRCUIT	4
	2.2 WORKING PRINCIPLE	8
<b>3</b>	<b>COST OF THE COMPONENTS</b>	<b>10</b>
<b>4</b>	<b>RESULT AND DISCUSSION</b>	<b>11</b>
	4.1 WORKING MODEL	11
	4.2 ADVANTAGES	12
	4.3 LIMITATIONS	12
	4.4 APPLICATIONS	12
	4.5 FUTURE ENHANCEMENT	12
<b>5</b>	<b>CONCLUSION</b>	<b>13</b>



# **CHAPTER 1**

## **PROBLEM STATEMENT**

The increasing need for covert audio surveillance and monitoring in applications such as security systems, crime investigations, and wildlife studies necessitates the development of a reliable and efficient listening device. Traditional solutions are often bulky, power-intensive, or lack sufficient sensitivity to capture clear audio signals.

This project aims to design and implement a compact listening bug using an operational amplifier (op-amp), capable of amplifying faint sound signals for effective audio monitoring. The system should ensure high sensitivity to weak acoustic signals, low power consumption, and minimal noise interference. It should also include provisions for long-distance transmission of audio signals or storing them for later analysis.

The challenges include selecting an appropriate op-amp configuration, designing a low-noise preamplifier circuit, ensuring proper filtering to eliminate unwanted frequencies, and achieving an optimal balance between power efficiency and audio quality.

The proposed system is designed to address specific problems:

### **1.1 WEAK SIGNAL AMPLIFICATION:**

Capturing faint audio signals from a distant or low-intensity sound source is a primary challenge. Microphones generate very weak electrical signals that are often inadequate for direct processing or transmission. The listening bug circuit must include an op-amp configuration with high gain to amplify these signals to a usable level.



## **1.2 NOISE REDUCTION AND SIGNAL CLARITY**

Ambient noise and interference from electronic components can corrupt the desired audio signals, making it challenging to extract clear audio. The circuit must be designed to minimize noise through careful selection of components and proper grounding. Additionally, integrating low-pass or band-pass filters can help eliminate unwanted frequencies.

## **1.3 POWER EFFICIENCY AND PORTABILITY**

Listening devices are often deployed in remote or covert locations where access to power is limited. Designing the circuit to operate efficiently on a low-voltage power source, such as a battery, is crucial. The circuit must strike a balance between power consumption and performance, ensuring reliable operation for extended periods without frequent battery replacements or recharging.

## **1.4 COMPACTNESS AND DURABILITY**

The listening bug circuit needs to be small and lightweight to allow for easy concealment and portability. Achieving this compactness while ensuring robust performance is a key challenge. Furthermore, the circuit must be designed to withstand environmental conditions such as temperature variations and humidity, ensuring consistent performance in diverse operating environments.

## **1.5 BACKGROUND OF THE WORK**

Listening devices, often referred to as "bugs," have been a significant area of research and development in the fields of surveillance, security, and audio processing. These devices are designed to capture faint sound signals from the environment or specific sources and amplify them for further analysis, transmission, or recording. Over the years, advancements in electronics have led to the miniaturization of components, making it feasible to create compact and efficient listening devices.

The use of operational amplifiers (op-amps) in audio applications is well-established due to their versatility and high gain. Op-amps are particularly effective in designing preamplifiers for audio systems, as they can amplify weak signals from microphones with minimal distortion. Various circuit topologies, such as inverting and non-inverting configurations, have been utilized to optimize the gain and noise characteristics of op-amp-based amplifiers.

In the context of listening bug circuits, the focus has traditionally been on achieving high sensitivity, low noise, and efficient power consumption. Modern designs often integrate additional components, such as filters for frequency selection and wireless modules for signal transmission, to enhance functionality. However, challenges remain in balancing these features with the need for compactness, durability, and long operational life.

This project builds on these developments by leveraging the capabilities of an op-amp to design a listening bug circuit that addresses key challenges, such as signal amplification, noise reduction, and power efficiency. The proposed design aims to provide a reliable and robust solution for covert audio monitoring in various applications.

## CHAPTER 2

### DESIGN PROCEDURE OF BUG CIRCUIT

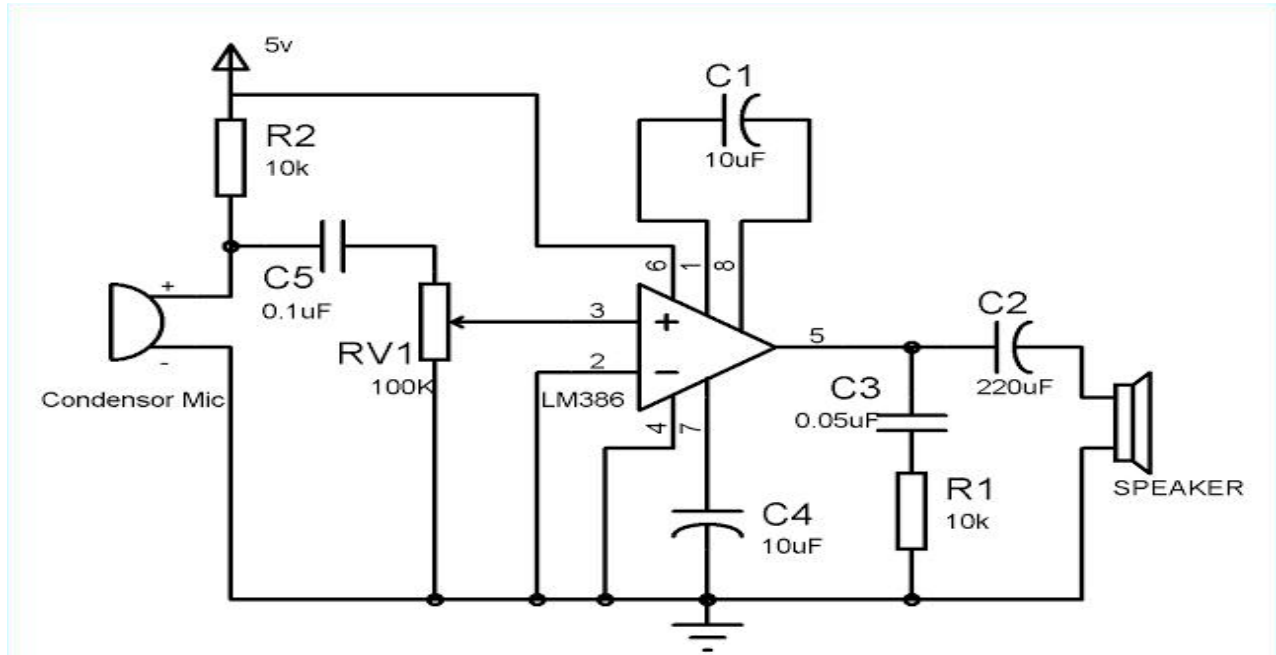


Figure 2.1 Circuit Diagram of Listening Bug circuit

#### 2.1 CIRCUIT DESIGN OF BUG CIRCUIT

The circuit is divided into six main components. They are : 10k $\Omega$ , 100k $\Omega$  resistors, 100  $\Omega$  variable resistor, 0.2 uf, 470 uf, 250 uf capacitor, 2N2222(NPN), 2N2907(PNP) Transistors, microphone and a 4  $\Omega$  speaker above the figure represented.

##### 2.1.1 IC LM386

The IC LM386 is a widely used general-purpose operational amplifier (op-amp) that features high input impedance, low output impedance, and a wide bandwidth. It has a single supply voltage range and is commonly used in amplifying weak signals in analog circuits. Its internal design includes differential inputs, which make it ideal for many linear applications, such as filters and voltage followers. The IC LM386 is known for its ease of use and reliability in various audio, signal processing, and feedback systems. It operates with a low noise level, making it suitable for precise applications.

### 2.1.2 100 kΩ RESISTOR

The 100 kΩ resistor is a fixed resistor primarily used to set the gain of the circuit. When used with the LM386 IC, it is typically placed in the feedback loop to control the amount of amplification applied to the input signal. By stabilizing the gain, it prevents over-amplification, which could lead to distortion. Additionally, it may be used in biasing networks to ensure that the active components like transistors or ICs operate at their optimal point, ensuring consistent performance across varying input levels. This resistor is crucial for maintaining signal clarity and stability in the circuit.

### 2.1.3 10 kΩ RESISTOR

In a listening bug circuit, a 10k ohm resistor is often used to set the gain in op-amp configurations, control input impedance, and assist in biasing components like transistors. It can also help stabilize the circuit and prevent distortion, ensuring clean signal amplification and reliable operation.

### 2.1.4 0.1 μF CAPACITOR

The **0.1 μF capacitor** is another ceramic capacitor that works similarly to the 0.05 μF capacitor but is often used to filter slightly lower-frequency noise. When used together, these capacitors form a robust noise-filtering network, ensuring that both high and medium-frequency noise are removed from the power supply and signal lines. This capacitor is crucial for achieving high fidelity in the audio signal and ensuring the circuit operates smoothly under varying conditions.

### 2.1.5 220 μF CAPACITOR

In a listening bug circuit, a 220 μF capacitor is used for power supply filtering and decoupling, helping to stabilize voltage and reduce noise or ripple. This ensures smooth operation of the operational amplifier and other components. It can also be used for signal coupling, blocking DC components while allowing the desired audio signal to pass through for amplification.

### **2.1.5 0.1 $\mu$ F Capacitor**

The **0.1  $\mu$ F capacitor** is another ceramic capacitor that works similarly to the 0.05  $\mu$ F capacitor but is often used to filter slightly lower-frequency noise. When used together, these capacitors form a robust noise-filtering network, ensuring that both high and medium-frequency noise are removed from the power supply and signal lines. This capacitor is crucial for achieving high fidelity in the audio signal and ensuring the circuit operates smoothly under varying conditions.

### **2.1.6 0.05 $\mu$ F CAPACITOR**

In a listening bug circuit, a 0.05  $\mu$ F capacitor is commonly used for signal coupling or decoupling. It blocks DC components while allowing AC audio signals to pass through, ensuring proper signal flow between stages. Additionally, it can act as a filter, reducing noise or stabilizing the power supply for reliable operation.

### **2.1.7 MICROPHONE**

In a listening bug circuit, the microphone converts ambient sound into a weak electrical signal. It captures sound with varying sensitivity, depending on the type of microphone used. The signal is then amplified by components like op-amps or transistors, as the mic signal is too weak for processing. The frequency response of the mic determines the range of sounds it can pick up. Proper positioning and concealment of the microphone are essential for effective, undetectable operation in a listening bug system.

### **2.1.8 SPEAKER $4\Omega$**

In a listening bug circuit, the speaker converts the amplified electrical signal back into audible sound. It must match the circuit's impedance for efficient power transfer. The speaker should handle the appropriate power without distortion, ensuring clear output. A small, portable speaker is often used for discreetness and convenience. The speaker's frequency range should align with the captured audio to accurately reproduce sounds, such as speech or environmental noises.

### **2.1.9 Audio Jack**

The audio jack acts as the interface for connecting external microphones or audio input devices to the circuit. It ensures that the input signal is transferred efficiently to the amplifier for processing. Depending on the design, it may support mono or stereo connections and provide a convenient way to integrate various audio sources into the listening bug. The audio jack is indispensable for feeding the circuit with external audio signals.

### **2.1.10 Breadboard**

The breadboard is used as a platform for assembling and testing the listening bug circuit without the need for soldering. It allows components to be easily inserted, connected, and modified, making it ideal for prototyping and debugging. By using a breadboard, you can experiment with different circuit configurations and quickly make changes, ensuring the design is functional before final assembly.

### **2.1.11 Connecting Wires**

The connecting wires establish electrical connections between components on the breadboard. They carry power, ground, and signal paths throughout the circuit, ensuring seamless operation. High-quality wires with proper insulation are critical to avoid short circuits and maintain reliable connections during testing and operation. These wires are indispensable for completing the circuit and facilitating its operation.

## 2.2 WORKING PRINCIPLE

The listening bug circuit is an electronic system designed to capture, amplify, and either output or transmit audio signals, often used in surveillance applications. The process begins with a microphone, which serves as the primary sensor for capturing sound from the environment. When sound waves, such as a conversation or background noise, hit the microphone's diaphragm, it vibrates and converts these mechanical vibrations into a very weak electrical signal. This electrical signal, though a representation of the sound, is typically too faint to be useful and must be amplified for further processing.

Once the microphone captures the sound, the weak electrical signal is sent to an operational amplifier (commonly the IC 741), which plays a key role in increasing the signal's voltage while maintaining its original quality. The amplifier is configured in such a way that the input signal's amplitude is increased without altering the sound's properties. The amount of amplification is determined by feedback resistors and often a potentiometer, which allows for adjustable gain, ensuring that the audio signal is amplified to a usable level without introducing distortion. The gain control is important for preventing clipping (when the signal becomes too loud and distorts) or inaudibility (if the signal is too quiet).

Further signal processing is often employed to improve the quality of the audio. Filters built with capacitors and resistors are used to remove unwanted noise or frequencies. For example, a low-pass filter might be used to eliminate high-frequency noise, while a high-pass filter removes low-frequency hums or static. These filters help to clean up the signal, ensuring it remains clear and accurate, especially in environments with external interference.

Once the audio signal is amplified and filtered, additional power amplification may be necessary to drive a speaker or transmitter. While the operational amplifier boosts the signal's voltage, a transistor or other power amplifier is typically used to increase the signal's current, making it strong enough to either power a speaker or transmit wirelessly over a distance. The transistor—typically an NPN or PNP type—amplifies the current, allowing for output to either a speaker or a wireless transmitter.

In some designs, the signal is transmitted wirelessly via an RF transmitter, which modulates the audio signal onto a carrier frequency for long-range transmission. The final output stage involves converting the electrical signal into audible sound. A speaker performs

this task by using electromagnetism, causing its diaphragm to vibrate in response to the audio signal and producing sound waves.

Power supply stability is a key aspect of the circuit. Capacitors are used to smooth out fluctuations in the voltage supply, preventing distortions in the amplified signal. Decoupling capacitors placed near integrated circuits (ICs) help minimize noise from power lines, ensuring the signal remains clear throughout the amplification process.

In summary, the listening bug circuit integrates microphones, operational amplifiers, resistors, capacitors, transistors, and speakers to create a functional surveillance system. Its design allows for flexible use in a range of applications, from simple audio monitoring to more advanced covert surveillance systems, all while ensuring minimal distortion, noise, and power consumption.





## CHAPTER 3

### COST OF COMPONENTS

Table 3.1 Cost and Quantity of the Components

COMPONENT	QUANTITY	COST (APPROX.)
100 k Resistor	1	3
10 k Resistor	1	2
100 k Variable resistor	1	3
10 $\mu$ F Capacitor	2	14
220 $\mu$ F Capacitor	1	7
0.05 $\mu$ F Capacitor	7	7
0.1 $\mu$ F Capacitor	1	7
IC LM386	1	32
Audio jack	1	40
Speaker 4 $\Omega$	1	110
Breadboard	1	85
Connecting Wires	As Required	24

GSTIN : 33BLRPS3239J1ZL Cell : 94433 03380

**BSL**

**ELECTRONICS & PROJECTS CENTER**

No.51, SUPER BAZZAR, TRICHY - 620 008.

No. **2726** Date: **12.11.24**

Name : .....

S.No.	Particulars	Qty.	AMOUNT	
			Rs.	Ps.
	Speaker -	1	110	-
	mic	1	30	-
	LM386	1	32	-
	Breadboard	1	85	-
	Resistor	5	5	-
	Capacitor	5	35	-
	Battery	1	25	-
	Connect	1	24	-
	Wires	1	24	-
	<b>TOTAL</b>		<b>358</b>	<b>177</b>

For **BSL ELECTRONICS & PROJECTS CENTER**

## CHAPTER 4

### RESULT AND DISCUSSION

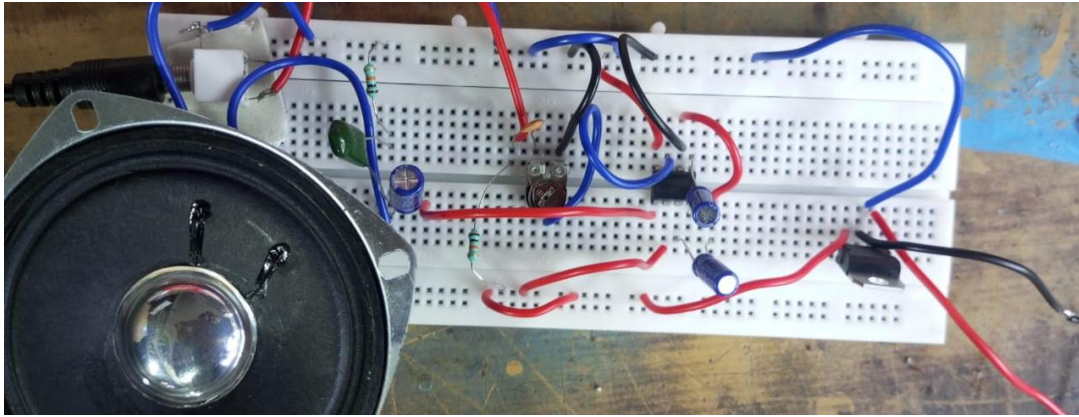


Figure 4.1 Working Model of Listening Bug Detector

#### 4.1 WORKING MODEL

The working model of the listening bug circuit begins with the microphone, which detects ambient sound and converts it into a weak electrical signal. This signal is then sent to an operational amplifier (IC 741), which boosts the signal's strength using resistors to control gain. The signal may be further cleaned with filters (capacitors and resistors) to remove unwanted noise. Once amplified, the signal is either output directly to a speaker for audible monitoring or transmitted via an RF transmitter for remote listening. The power stage, which uses transistors, ensures the signal is strong enough to drive the output stage, whether a speaker or transmitter. Additional components like capacitors help stabilize the power supply, ensuring smooth operation.

The Listening Bug Circuit functions by capturing audio from the surrounding environment using a microphone, amplifying the weak signal through operational amplifiers and transistors, and then either outputting the sound through a speaker or transmitting it wirelessly to a remote receiver.

The microphone picks up sound waves, which are converted into electrical signals. These signals are then amplified to an audible or transmissible level. The gain of the amplifier can be adjusted using resistors and a potentiometer to ensure the signal is not too weak or too

distorted. Filters may be used to remove noise, and additional power amplification is provided to drive a speaker or enable transmission. The audio can either be heard directly via the speaker or transmitted via a radio frequency (RF) transmitter for remote surveillance.

## **4.2 ADVANTAGE**

The listening bug circuit offers advantages like compact design for discreet use, effective amplification of weak audio signals, and the ability to filter noise for clear sound. It supports wireless transmission for remote monitoring and is versatile, finding applications in surveillance, research, education, and entertainment with minimal power consumption.

## **4.3 LIMITATIONS**

The listening bug circuit has limitations like restricted transmission range, high power consumption reducing battery life, susceptibility to signal interference causing noise or distortion, and potential audio quality degradation. Additionally, ethical and legal issues arise from unauthorized use, making its application controversial in many jurisdictions.

## **4.4 APPLICATIONS**

The listening bug circuit is used in surveillance for monitoring audio, in research for acoustic studies, and in education to teach amplification and transmission concepts. It also has applications in entertainment, such as toys and gadgets, where it enables audio playback or recording, showcasing its versatility in different fields.

## **4.5 FUTURE ENHANCEMENT**

Future limitations include potential detection by advanced security systems, stricter legal and ethical regulations restricting its use, and challenges in keeping up with modern communication technologies. Traditional designs may become outdated, requiring upgrades to match new standards in audio quality, power efficiency, and wireless transmission capabilities.

## **CHAPTER 5**

### **CONCLUSION**

The listening bug circuit provides a practical and versatile solution for audio surveillance, offering the ability to capture, amplify, and output or transmit audio in a variety of environments. While the circuit can be easily miniaturized and concealed, making it ideal for covert applications, it also faces challenges related to power consumption, signal interference, and audio quality. Despite these limitations, its wide range of applications—ranging from security to wildlife monitoring—demonstrates its value. Future advancements in wireless transmission, miniaturization, and digital processing could further enhance the functionality and usability of the listening bug circuit, making it an even more effective tool for audio surveillance.